



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM I) THEORY EXAMINATION 2023-24**  
**BASIC ELECTRICAL ENGINEERING**

TIME: 3HRS

M.MARKS: 100

**Note:** 1. Attempt all Sections. If require any missing data; then choose suitably.

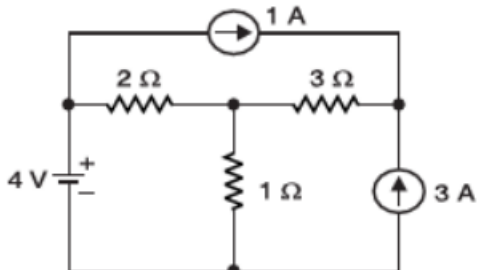
**SECTION A**

**1. Attempt all questions in brief.**

Q no.	Question	Marks	CO
a.	Give the statement of thevenin's theorem.	2	1
b.	Explain active and passive elements with examples.	2	1
c.	What is the rms and average value of sinusoidal voltage.	2	2
d.	Define resonance in series RLC circuit.	2	2
e.	Explain the types of losses in transformer.	2	3
f.	What are ferromagnetic materials. Give their properties.	2	3
g.	Why single phase induction motor is not self starting.	2	4
h.	What are the starting methods of synchronous motor.	2	4
i.	Explain switchgear and its need in electrical systems?	2	5
j.	Explain the function of SFU?	2	5

**SECTION B**

**2. Attempt any three of the following:**

Q no.	Question	Marks	CO
a.	Using mesh analysis, find current in $2\ \Omega$ resistor in the circuit shown in figure below: 	10	1
b.	Derive the Bandwidth, Lower half power frequency, Upper half power frequency of series resonant RLC circuit.	10	2
c.	(i) Derive the emf equation of a transformer. (ii) Draw the phasor diagram of ideal transformer at no load condition.	10	3
d.	Derive the emf equation of DC machine. Also give the types of DC generators.	10	4
e.	Describe the operating principle of MCB and ELCB in details with necessary circuit diagrams.	10	5

**SECTION C**

**3. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	Using thevenin's theorem find the current in $20\ \Omega$ resistance in the circuit.	10	1



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM I) THEORY EXAMINATION 2023-24**  
**BASIC ELECTRICAL ENGINEERING**

TIME: 3HRS

M.MARKS: 100

b.	<p>Find the current in 8 Ω resistance using superposition theorem.</p>	10	1

**4. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	Consider an electrical circuit shown in Figure. Determine (i) the current and power consumed in each branch (ii) the supply current and power factor. 	10	2
b.	Derive the relation between line and phase voltages for a delta-connected 3-φ balanced system. A balanced star-connected load of (10+j8) Ω/phase is connected to 3-φ, 440 V supply. Calculate line current, power factor, and power drawn by it.	10	2

**5. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	Explain the working of a single, phase transformer with suitable diagram. Draw the complete equivalent circuit model of a real transformer.	10	3
b.	A 50 kVA, 2000/200V transformer has full load copper & iron losses of 1.8 kW & 1.5 kW respectively. Figure out: <ol style="list-style-type: none"> <li>The efficiency at half load &amp; at unity power factor.</li> <li>The efficiency at full load &amp; at 0.8 power factor lagging.</li> <li>Maximum efficiency and the load corresponding to max. efficiency</li> </ol>	10	3



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM I) THEORY EXAMINATION 2023-24**  
**BASIC ELECTRICAL ENGINEERING**

TIME: 3HRS

M.MARKS: 100

**6. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	An 8-pole, 400V shunt motor has 960 wave connected armature conductors. The full load armature current is 40A and flux per pole is 0.02Wb. The armature resistance is $0.1\Omega$ and the contact drop is 1V per brush. Calculate the full load speed of the motor.	10	4
b.	Draw and explain Torque-slip characteristics of 3-phase induction motor. A 3-phase, 4 pole induction motor is supplied from 3-phase, 50 Hz ac supply. Determine: Synchronous speed, rotor speed when slip is 4% and rotor frequency.	10	4

**7. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	(i) Write short notes on cables (ii) Write short notes on types of batteries	10	5
b.	Explain the need of earthing of electrical equipment. What are the different methods of earthing.	10	5