

B. Tech.
(SEM I) THEORY EXAMINATION 2022-23
EMERGING DOMAIN IN ELECTRONICS ENGINEERING

Time: 3 Hours

Total Marks: 100

Note: Attempt all Sections. If you require any missing data, then choose suitably.

SECTION A

1. Attempt all questions in brief.

2*10 = 20

(a)	What is PIV of Half wave and Full wave bridge rectifier.
(b)	Calculate the reverse saturation current of a diode if the current at 0.4V forward bias is 0.2 mA at room temperature and the ideality factor is 2.
(c)	How FET differs from the BJT?
(d)	Calculate the value of transconductance (gm) for a JFET, IDSS=12mA, VP = -3V at a bias point of VGS = -2V
(e)	What is the difference between microprocessor and microcontroller?
(f)	The output of a particular OPAMP increases 10V in 15μs. What is the slew rate?
(g)	Write down the truth table of 3 input X-NOR gate.
(h)	State De Morgan's Law.
(i)	A broadcast radio transmitter radiates 15KW when the modulation percent is 70. How much is the carrier power?
(j)	Define Satellite communication.

SECTION B

2. Attempt any three of the following:

10*3 = 30

(a)	(i) Write short notes on: LED and LCD. (ii) Define the various components of IOT system with neat block diagram.
(b)	Draw and explain the common emitter (CE) circuit of a bipolar junction transistor. Sketch its output and input characteristics. Indicate the region of operation on output characteristics.
(c)	Explain unity gain OP-AMP. With suitable circuit diagram obtain the expression for integrator and differentiator OP-AMP.
(d)	(i) $(BDA.C)_{16} = ()_{10}$ (ii) $(1110111)_2 = ()_8$ (iii) Perform $(1011)_2 - (101)_2$ using 2's complement method. (iv) $(225)_X = (341)_8$, Find the value of X. (v) $(78.25)_{10} = ()_2$
(e)	(i) Explain the amplitude modulation. Obtain an expression for an AM wave sinusoidal modulation.

	(ii) The antenna current of an AM broadcast transmitter, modulated to a depth of 40 percent by an audio sine wave, is 11A. It increases to 12A as a result of simultaneous modulation by another sine wave. What is the modulation index due to second wave.
--	--

SECTION C

3. Attempt any one part of the following: 10*1 = 10

(a)	(i) Draw the circuit diagram and explain the working of a full wave bridge rectifier circuit. (ii) Define Static and Dynamic resistance of PN junction diode? Obtain the mathematical expression for the Dynamic resistance (r_{ac}).
(b)	(i) Draw and explain the operation of center tapped full wave rectifier with input and output waveforms. Calculate ripple factor. (ii) Determine the output V_0 for the given network.

4. Attempt any one part of the following: 10 *1 = 10

(a)	Explain construction, working and characteristics of n-channel Depletion MOSFET. Distinguish between D-MOSFET and E-MOSFET..
(b)	What is voltage multiplier? Draw and explain the circuit diagram of halfwave voltage Doubler. How can you construct voltage Tripler and Quadrupler?

5. Attempt any one part of the following: 10*1 = 10

(a)	(i) Define an operational amplifier? Draw its block diagram. Draw the transfer characteristics. (ii) Determine the output voltage (V_0) for the given circuit, where $V_1 = 10V$ and $V_2 = 5V$
-----	--

(b)	<p>(i) Enlist the characteristics of OP-AMP. Obtain the expression for voltage gain in non-inverting OP-AMP.</p> <p>(ii) Calculate the output voltage for the given circuit, resistance value if $R_f = 470\text{K}\Omega$, $R_1 = R_2 = R_3 = 33\text{K}\Omega$ for input voltage of 5mV.</p>

6. Attempt any *one* part of the following: 10*1 = 10

(a)	<p>(i) What are universal Gates.</p> <p>(ii) Construct the two input XOR gate by using only NAND gates</p>
(b)	<p>Simplify the given expression and implement this NOR gate only. $F(A, B, C, D) = \Pi(1,3,4,5,6,7,11,12,14,15)$. $d(2,9,10,13)$</p>

7. Attempt any *one* part of the following: 10*1 = 10

(a)	<p>An Audio frequency signal $10 \sin 2\pi \times 400t$ is used to amplitude modulate a carrier of $50 \sin 2\pi \times 10^5 t$. Calculate:</p> <p>(i) Modulation Index (ii) Amplitude of each side band</p> <p>(iii) Total power delivered to the load of $1\text{K}\Omega$</p> <p>(iv) Bandwidth</p> <p>(v) Transmission efficiency</p>
(b)	<p>(i) Sketch the block diagram of communication systems and explain the function of each system.</p> <p>(ii) Explain the evolution of mobile communication.</p>